

# Capacitive Overview

## Series Capacitive

$$X_{CT} = X_{C1} + X_{C2} + X_{C3}$$

$$I_{CT} = I_{C1} = I_{C2} = I_{C3}$$

$$E_{CT} = E_{C1} + E_{C2} + E_{C3}$$

$$\text{VAR}_{CT} = \text{VAR}_{C1} + \text{VAR}_{C2} + \text{VAR}_{C3}$$

$$C_T = \frac{1}{\frac{1}{C1} + \frac{1}{C2} + \frac{1}{C3}}$$

## Parallel Capacitive

$$X_{CT} = \frac{1}{\frac{1}{X_{C1}} + \frac{1}{X_{C2}} + \frac{1}{X_{C3}}}$$

$$I_{CT} = I_{C1} + I_{C2} + I_{C3}$$

$$E_{CT} = E_{C1} = E_{C2} = E_{C3}$$

$$\text{VAR}_{CT} = \text{VAR}_{C1} + \text{VAR}_{C2} + \text{VAR}_{C3}$$

$$C_T = C_1 + C_2 + C_3$$

## Series Resistive Capacitive

$$Z = \sqrt{R^2 + X_C^2}$$

$$I_T = I_R = I_C$$

$$E_T = \sqrt{E_R^2 + E_C^2}$$

$$VA = \sqrt{P^2 + \text{VAR}_C^2}$$




## Parallel Resistive Capacitive

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_C}\right)^2}}$$

$$I_T = \sqrt{I_R^2 + I_C^2}$$

$$E_T = E_R = E_C$$

$$VA = \sqrt{P^2 + \text{VAR}_C^2}$$

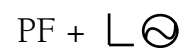


## Series Resistive Inductive Capacitive

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$I_T = I_R = I_L = I_C$$

$$E_T = \sqrt{E_R^2 + (E_L - E_C)^2}$$
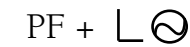
$$VA = \sqrt{P^2 + (\text{VAR}_L - \text{VAR}_C)^2}$$



## Parallel Resistive Inductive Capacitive

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}}$$

$$I_T = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$E_T = E_R = E_L = E_C$$

$$VA = \sqrt{P^2 + (\text{VAR}_L - \text{VAR}_C)^2}$$

